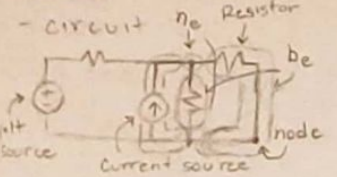


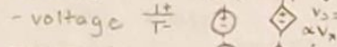

Principles of Electrical Engineering

Study Guide

Basics

- circuit 
 n_e = branches b then n_e
 n_e = node where 3+ elements join
 $L = b - n + 1$ (indep loops)
 mesh - loop does not have other loops inside


Sources

- voltage $\frac{1}{T}$ 
 - current 

Basics (cont)

- Current (A, Amp)
 $i(t) = \frac{d}{dt} q(t)$
 $q(t) = \int_{-\infty}^t i(x) dx + q(t_0)$
 - Voltage (V, Volts)
 $V = \frac{d}{dt} \phi$
 - Power (W, Watt, J/s)
 $P = \frac{d}{dt} W = iV$
 - Energy/Work (J)
 $W(T) = \int_0^T P(x) dx$
 - $p > 0 \rightarrow$ consume power
 - $p < 0 \rightarrow$ produce power
 * $Z_{in} = \text{constant}$
 $P_{generated} = P_{dissipated}$



Passive Elements

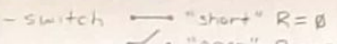- switch  "short" $R=0$
 "open" $R=\infty$
 - Resistance (Ω , ohm)
 $R = \frac{V}{I}$
 $V = IR$
 $P = iV = I^2 R = \frac{V^2}{R}$

Kirchoff

① walk around a loop
 ② Add elements
 + \rightarrow - depending on crossing
 $V \rightarrow + \rightarrow -$ is +
 $V \rightarrow - \rightarrow +$ is -
 $\# \text{ loops} = b - n + 1 = \# \text{ eqns}$


Equivalence

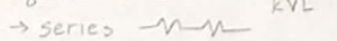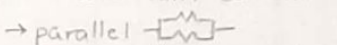\rightarrow series 
 $R_{eq} = R_1 + R_2 + \dots$
 \rightarrow constant current
 \rightarrow parallel 
 $R_{eq} = (\frac{1}{R_1} + \frac{1}{R_2} + \dots)^{-1}$
 \rightarrow constant voltage

ΔY
 $R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$
 $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$
 $R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$
 $R_1 = \frac{R_a R_b}{R_c}$
 $R_2 = \frac{R_a R_c}{R_b}$
 $R_3 = \frac{R_b R_c}{R_a}$

- voltage divider (series)
 $V_n = I R_n = V_{source} \frac{R_n}{R_{total}}$
 - w/ ∞ resistors
 - current divider (parallel)
 $I_n = I_s \frac{R_{total}}{R_n}$
 - multiple
 $I_n = I_s \frac{R_1 R_2 \dots R_n}{R_n}$

Wheatstone

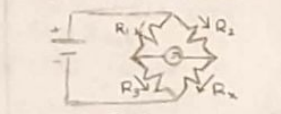\rightarrow used to find an unknown resistance

 $R_x = \frac{R_2 R_3}{R_1}$

Node Voltage

\rightarrow used to find an unknown resistance
 ① mark nodes
 ② indicate ground
 ③ write eqns from node-volt
 ie $V_1 \rightarrow -I_1 + \frac{V_1 - V_2}{R_1} = 0$
 $V_4 \rightarrow I_4 - \frac{V_4 - V_3}{R_3} = 0$
 ④ Constraints
 $V_1 - V_2 = V_3 - V_4$
 ⑤ Solve for node voltages
 * Solving for current/volt across elements
 ie $I_1 = \frac{V_1 - V_2}{R_1}$
 * Supernode (combine node volts) to simplify dep sources

Mesh Current

① Set up loops
 ② Eqns based on loops
 ie $-V_1 - R_1 I_1 + R_2 I_2 - R_3 (I_1 - I_2) = 0$
 $R_1 (I_1 - I_2) + I_3 = 0$
 ③ Constraints
 $I_3 = I_2$
 ④ Solve for current loops
 * Supermesh, walk 2 loops ignoring dep source


Source Transformation

$I_s = \frac{V}{R}$ or $V_s = I_s R$
 then current/voltage divider


Superposition


① Set all sources but 1 to be 0
 ② Calculate values for modified circuits
 ③ Repeat 1 & 2 for all sources
 ④ 2 values for each element = actual value


Operational Amplifiers

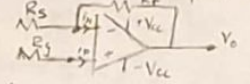
 $I_N = I_P = 0$ Amps
 $-V_{cc} \leq V_o \leq V_{cc}$
 $V_P = V_N$
 \rightarrow noninverting source \rightarrow + terminal
 $K = 1 + R_f/R_s$ gain
 \rightarrow inverting source \rightarrow - terminal
 $K = -R_f/R_s$ gain
 $V_o = K \cdot V_i$


\rightarrow rec use node volt to solve
 \rightarrow summing op amps
 multiple sources @ one terminal
 $V_o = -(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3)$
 \rightarrow Difference op amps
 source @ both terminals

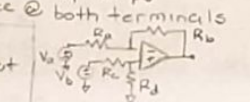

 $V_o = \frac{R_d(R_1 + R_2)}{R_a(R_3 + R_4)} V_1 - \frac{R_b}{R_c} V_2$
 if $\frac{R_b}{R_c} = \frac{R_d}{R_a}$, $V_o = \frac{R_d}{R_a} (V_1 - V_2)$
 \rightarrow buffer op amps
 $R_f = 0.5$
 avoid impedance
 \rightarrow Cascading
 $V_{in1} = \frac{V_{in2}}{A_1} = \frac{V_{in3}}{A_2} = \dots = \frac{V_{inN}}{A_N}$
 $V_{outN} = (A_1 A_2 \dots A_N) V_{in}$
 * Resistors can never be negative

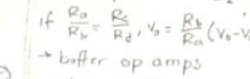
 $V_o = \frac{R_f}{R_i} V_i$
 $\delta = \frac{R_f}{R_i} \cdot \frac{R_f}{R_i} \cdot \frac{V_o}{V_i}$
 $V_o \approx \frac{R_f}{R_i} 2\delta \cdot V_i$

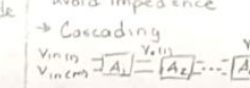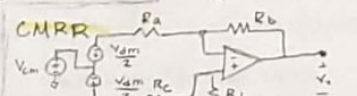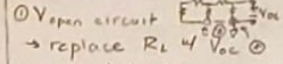
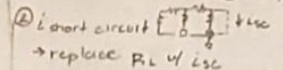

 $V_{in1} = \frac{V_{in2}}{A_1} = \frac{V_{in3}}{A_2} = \dots = \frac{V_{inN}}{A_N}$
 $V_{outN} = (A_1 A_2 \dots A_N) V_{in}$
 * Resistors can never be negative



Strain Gauge


 $V_o = \frac{R_L (ZAR)}{R_L^2 + (ZAR)^2} \cdot V_r$
 $\delta = \frac{R_L}{R} = \frac{R}{2R_1} \cdot \frac{V_o}{V_r}$
 $V_o \approx \frac{R_L}{R} 2\delta \cdot V_r$




 $A_{cm} = \frac{R_o R_d - R_i R_c}{R_o (R_c + R_d)}$
 $A_{dm} = \frac{R_i (R_o + R_d) + R_o (R_c + R_d)}{2R_o (R_c + R_d)}$ ideally ∞
 $CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$

Thevenin + Norton


① V open circuit 
 \rightarrow replace R_L w/ V_{oc}
 \rightarrow calculate w/ node volt
 ② I short circuit 
 \rightarrow replace R_L w/ I_{sc}
 \rightarrow calculate w/ node volt or mesh current
 ③ R_{eq}
 \rightarrow indep only
 \rightarrow replace R_L w/ a volt source
 \rightarrow ① = 1 & ② = 1
 \rightarrow Find R_{eq}
 \rightarrow w/ dep sources
 \rightarrow add volt source
 $V_T = IV$
 $\rightarrow R_{eq} = \frac{V_T}{I_T}$

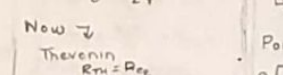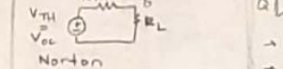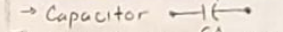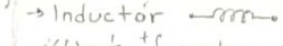Now \rightarrow
 Thevenin 
 V_{TH}
 V_{oc}
 Norton 
 V_N
 V_{oc}
 $\rightarrow P_L = V_{TH}^2 \left(\frac{R_L}{(R_L + R_{TH})^2} \right)$
 $P_{Lmax} = \frac{V_{TH}^2}{4R_{TH}} = \frac{I_N^2 R_{TH}}{4}$
 b/c max when $R_L = R_{TH}$

Inductance & Capacitor

\rightarrow Capacitor 
 $q(t) = C \cdot v(t) = \frac{C}{R} v(t)$
 $i(t) = C \frac{dv(t)}{dt}$
 $q(t) = \int_{-\infty}^t i(x) dx + q(t_0)$
 $w(t) = \frac{1}{2} C v^2(t) = \frac{q^2(t)}{2C}$
 $v(t) = \frac{1}{C} \int_{-\infty}^t i(x) dx + v(t_0)$
 \rightarrow Inductor 
 $i(t) = \frac{1}{L} \int_{-\infty}^t v(x) dx + i(t_0)$
 $w(t) = \frac{1}{2} L i^2(t)$
 $L = \frac{\mu N^2 A}{l}$
 $w(t) = \frac{1}{2} L i^2(t)$
 \rightarrow Inductor $\rightarrow i = I$ v=0
 capacitor $\rightarrow i=0$ v=V

Complex Numbers

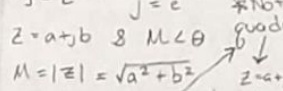$j = \sqrt{-1}$ so $j^2 = -1$
 $j = \cos 90^\circ + j \sin 90^\circ$
 $-j = \cos 270^\circ + j \sin 270^\circ$
 $Z = a + jb$ & $M \angle \theta$
 $M = |Z| = \sqrt{a^2 + b^2}$
 $\theta = \tan^{-1}(b/a)$
 $a = M \cos \theta$
 $b = M \sin \theta$
 $Z = a + jb$
 $Z^* = a - jb$
 $Z \cdot Z^* = |Z|^2 = M^2$
 $\angle 4 + A \rightarrow -90 \rightarrow -A + 90$
 \rightarrow complex conjugate
 $Z = a + jb \rightarrow Z^* = a - jb$
 $= M \angle \theta \rightarrow Z^* = M \angle -\theta$
 $Z \cdot Z^* = |Z|^2 = M^2$
 - phasor
 $A \cos(\omega t + \theta) = A \angle \theta$
 $= A \sin(\omega t + \theta - 90)$
 $\angle 4 + A \rightarrow -90 \rightarrow -A + 90$
 Impedance
 $-R \rightarrow Z_R = R \Omega$
 $-L \rightarrow Z_L = j\omega L \Omega$
 $-C \rightarrow Z_C = -j \frac{1}{\omega C} \Omega$
 * Then use regular circuit rules
 Phasor Power
 $S = IV^* \quad R = \frac{V_{RMS}^2}{S}$
 $\rightarrow S = \frac{V_{TH}^2}{2Z}$ not rms $S = P + jQ$
 Power Triangle

 $\rightarrow \theta_{pf} = -\cos^{-1}(pf)$ or $\cos^{-1}(pf)$
 $\rightarrow P = |S| \cos \theta$ Watts
 $\rightarrow Q = |S| \sin \theta$ VAR
 $P_{max} = \frac{V_{TH}^2}{4R} = \frac{V_{TH}^2}{4R}$
 $S_{source} + S_{line} + S_{load} = 0$